

Group Members

150460 - Makau Nathan Maganga

145768 - Ogato Deborah Kerubo

166326 - Muriithi Alvin

169648 - Kamau Joseph Manene

162437 - Ngigi Alex

150320 - Timothy Muigai


150767 - Leon Bundi

Experiment 1


The values measured using the multimeter match the values calculated based on the color code of the resistor using a web resource.

[resistor-calculator](#)

Resistor 1:

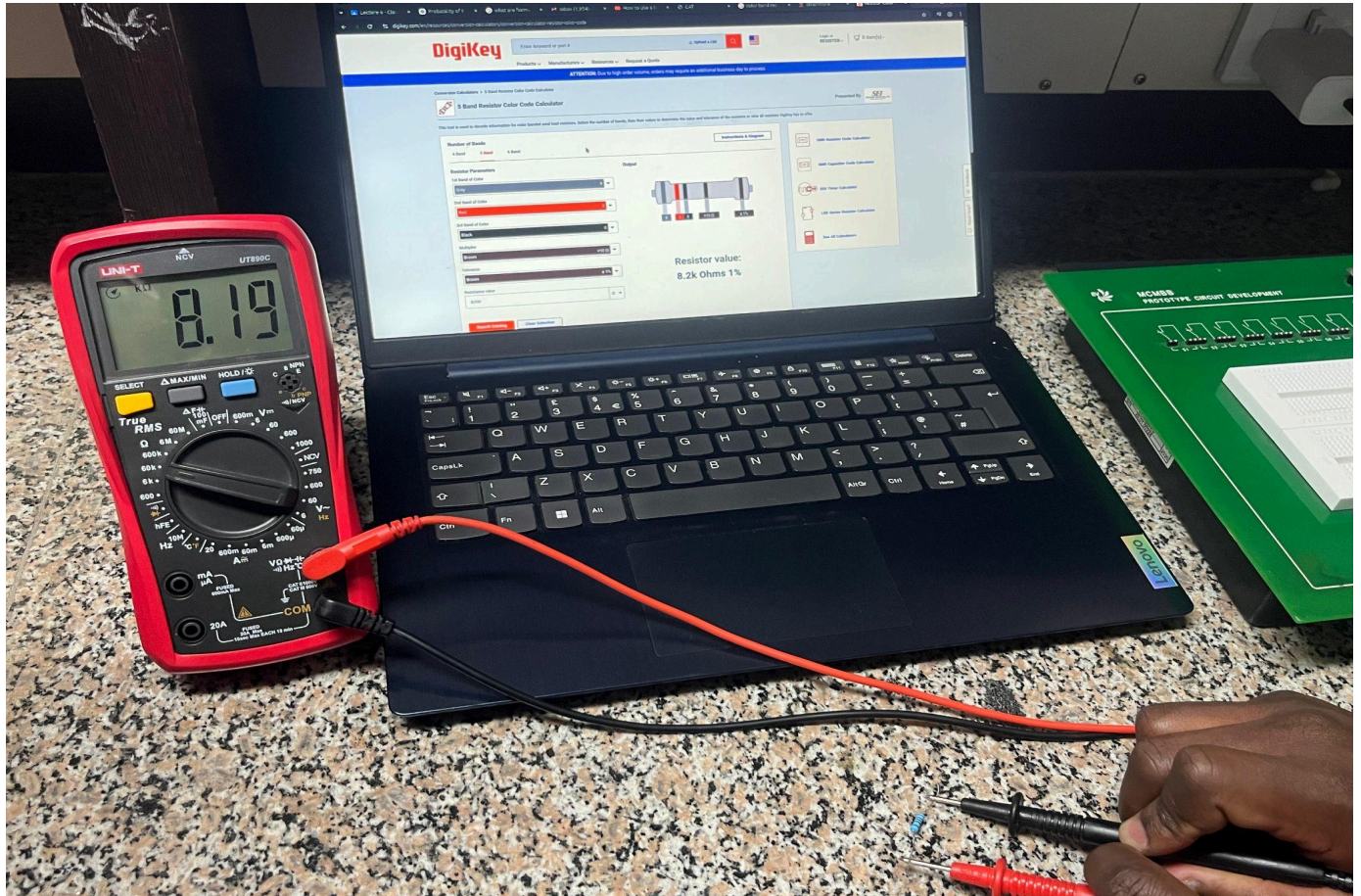

Resistor 2:

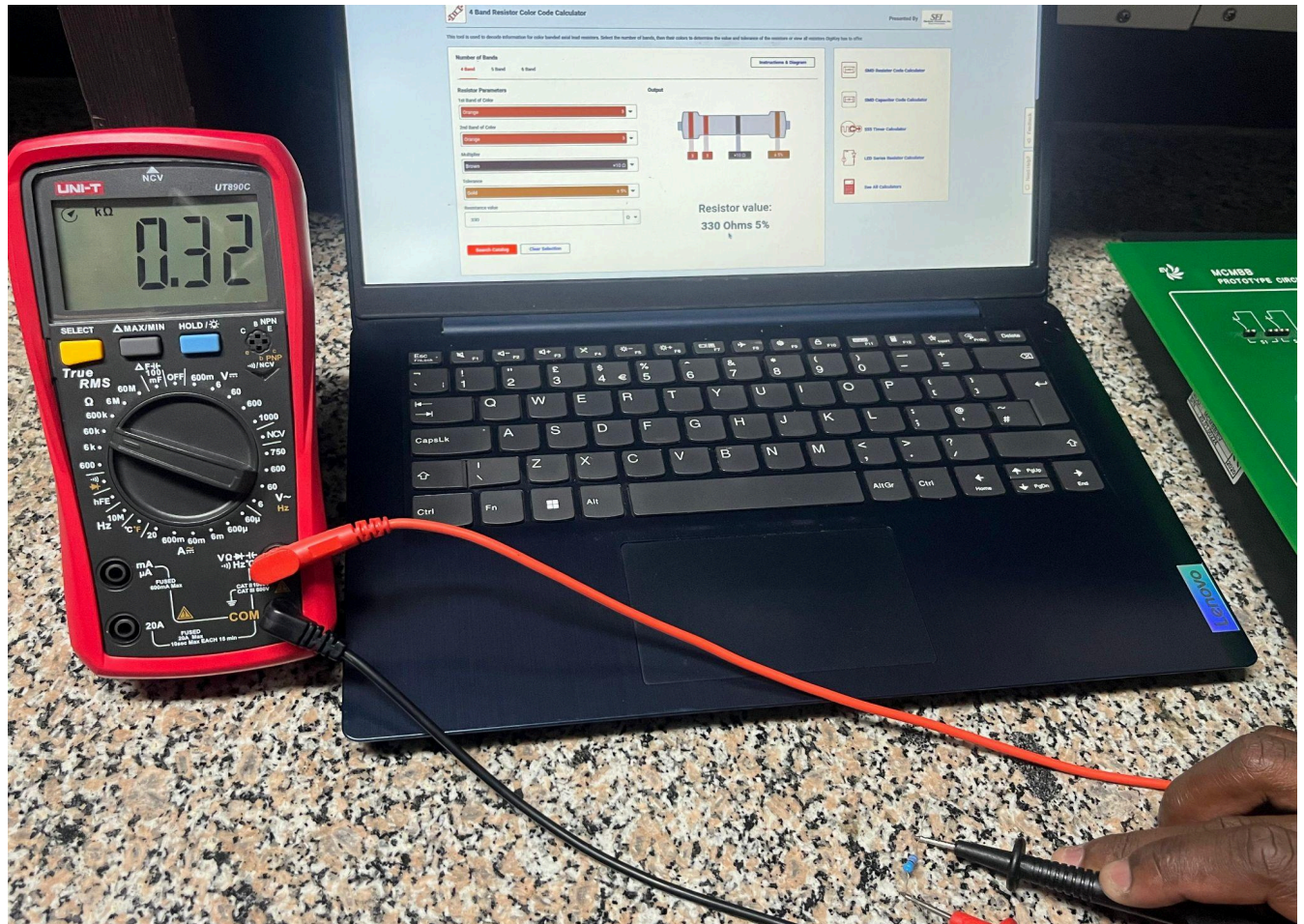


Experiment 2

Voltage of circuit with LED:




Pulse width modulation:


25%:

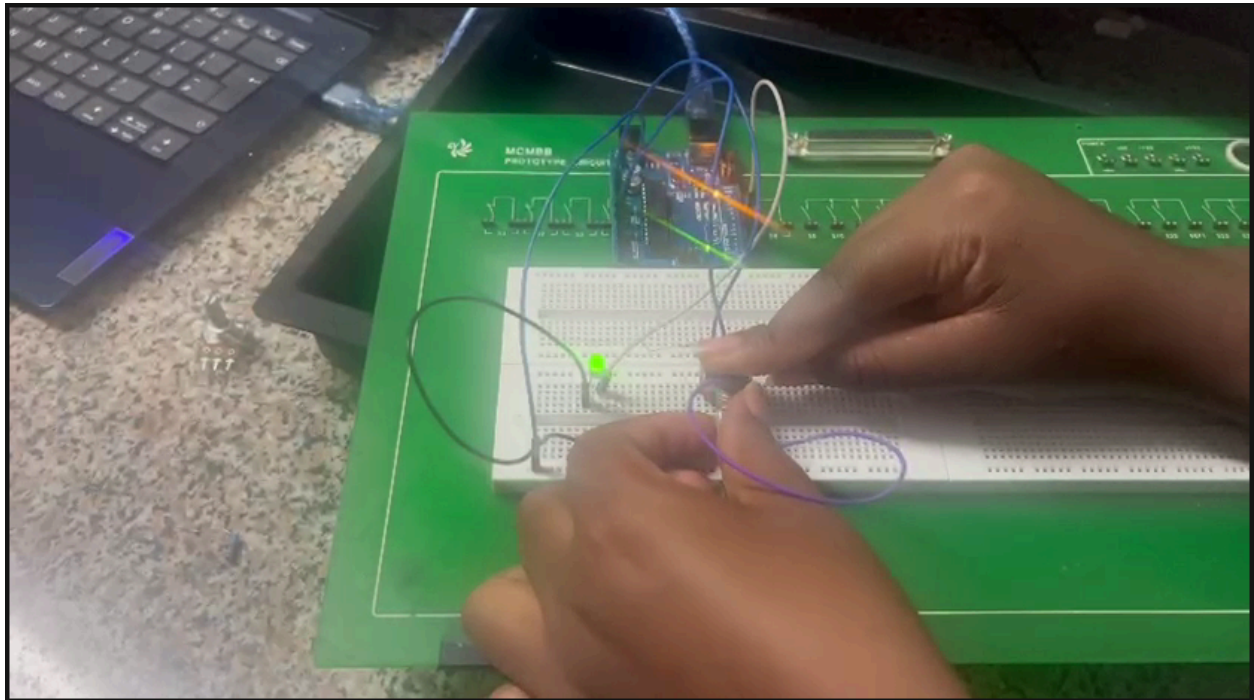

50%:

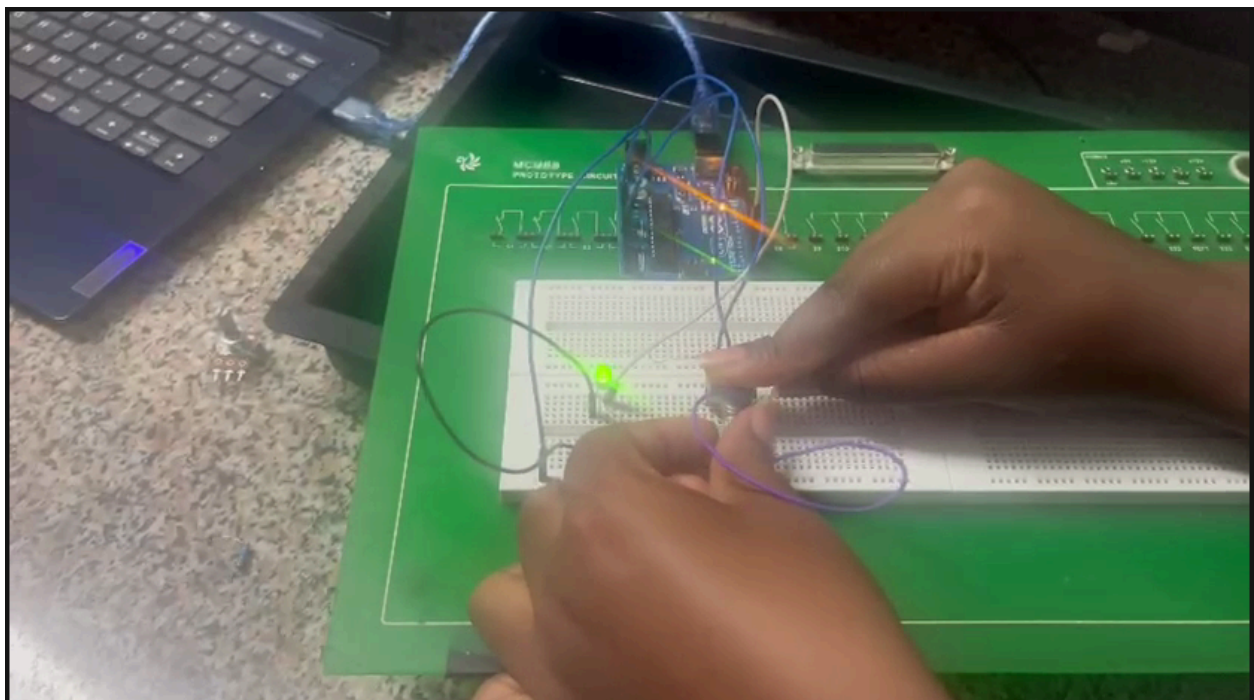


100%:

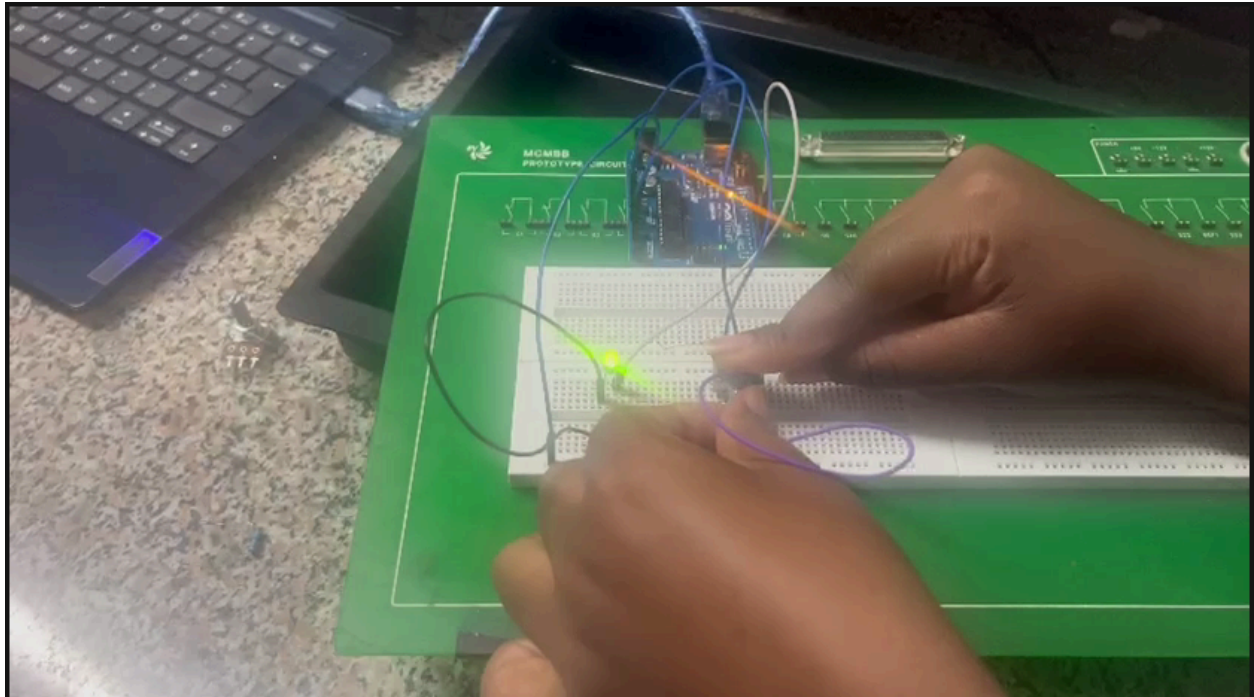


Experiment 3

Resistors in Series


Voltage across Resistor 1:

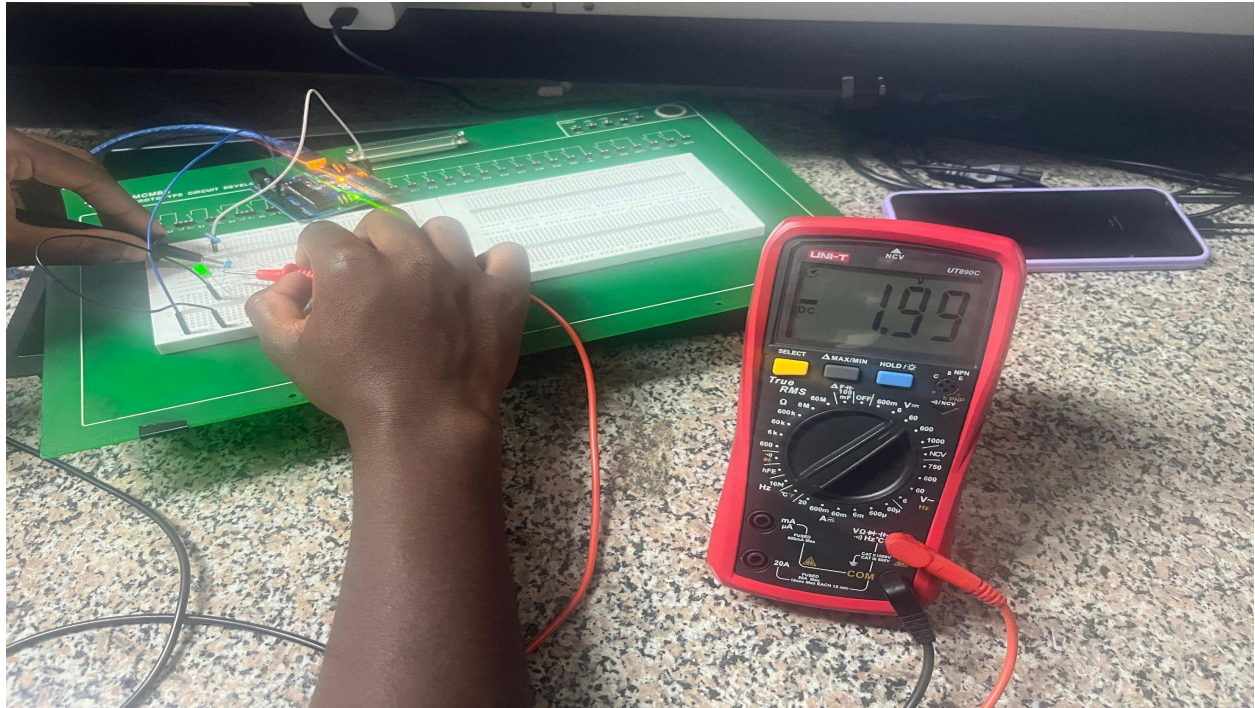

Voltage across Resistor 2:

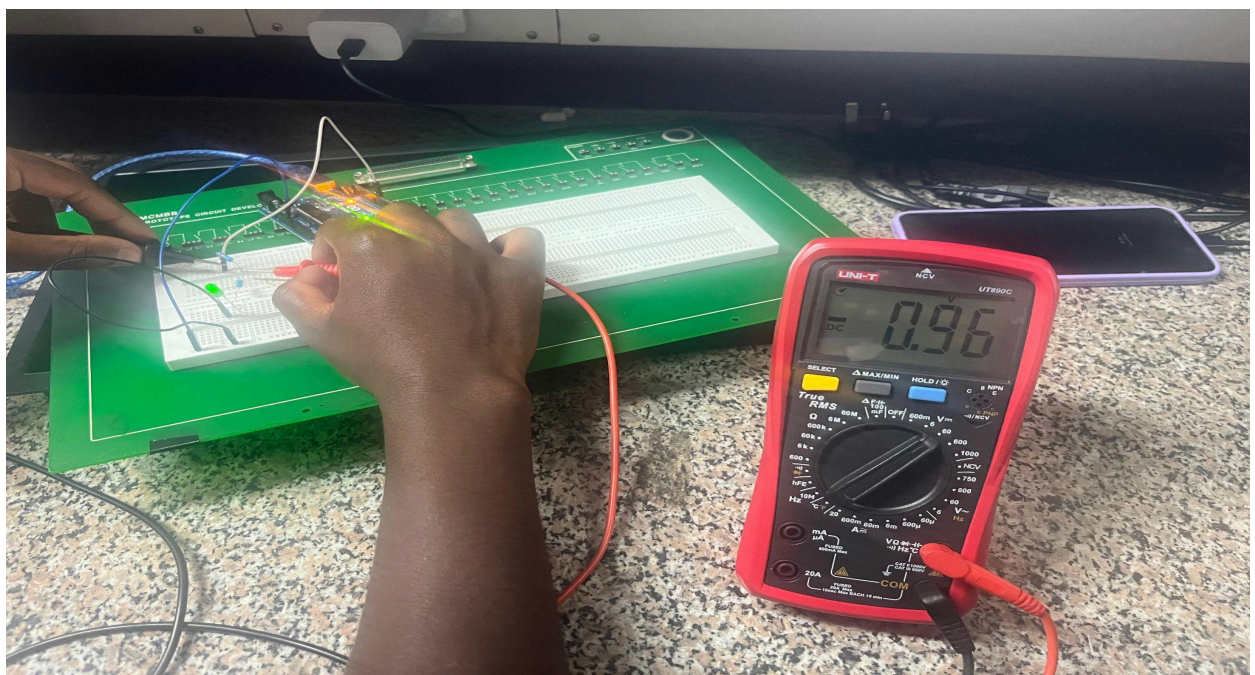


Total Voltage across the circuit(Voltage at R1 + Voltage at R2 = 1.99V + 0.96V = 2.95V):

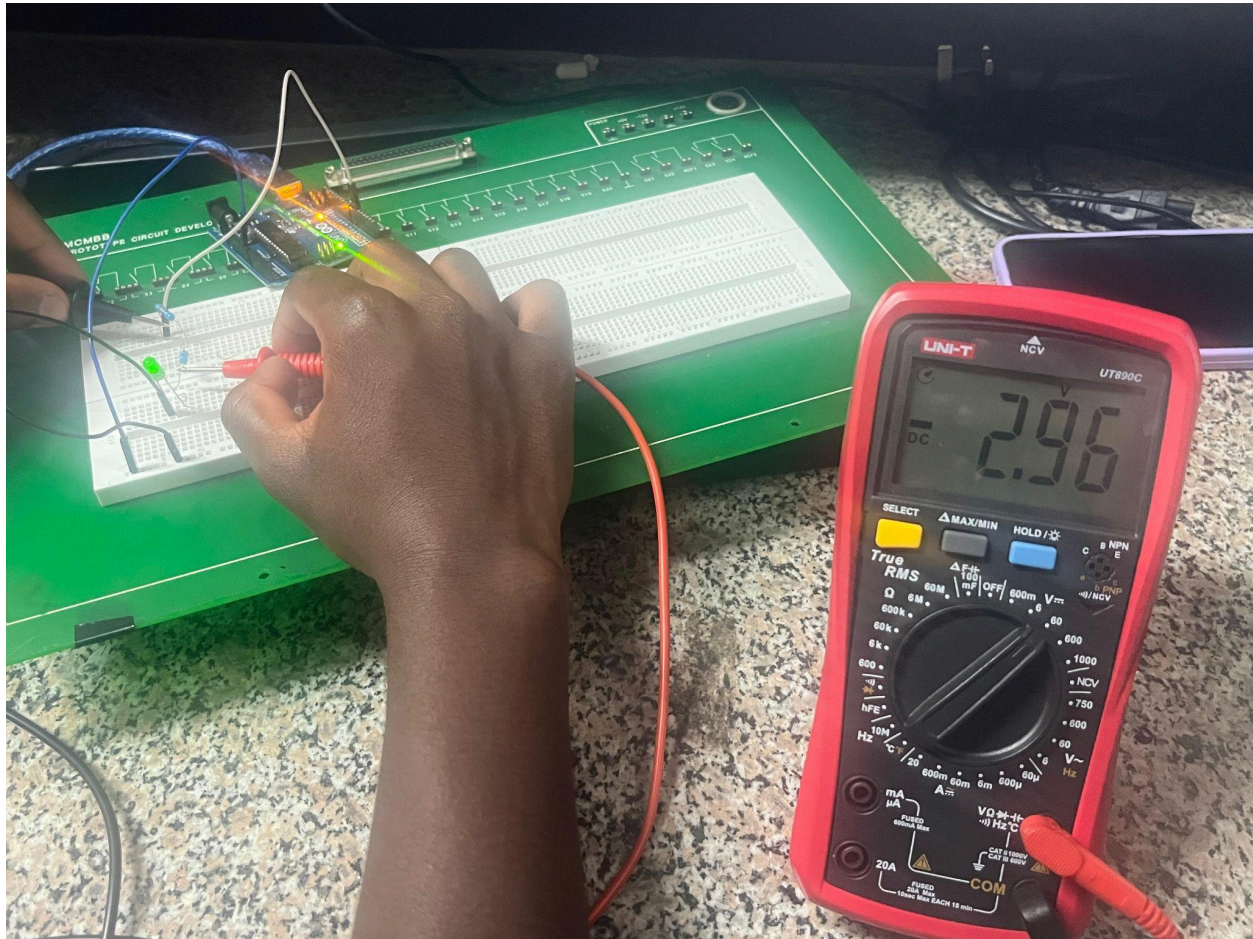


Experiment 4

Resistors in Parallel


Voltage across Resistor 1:

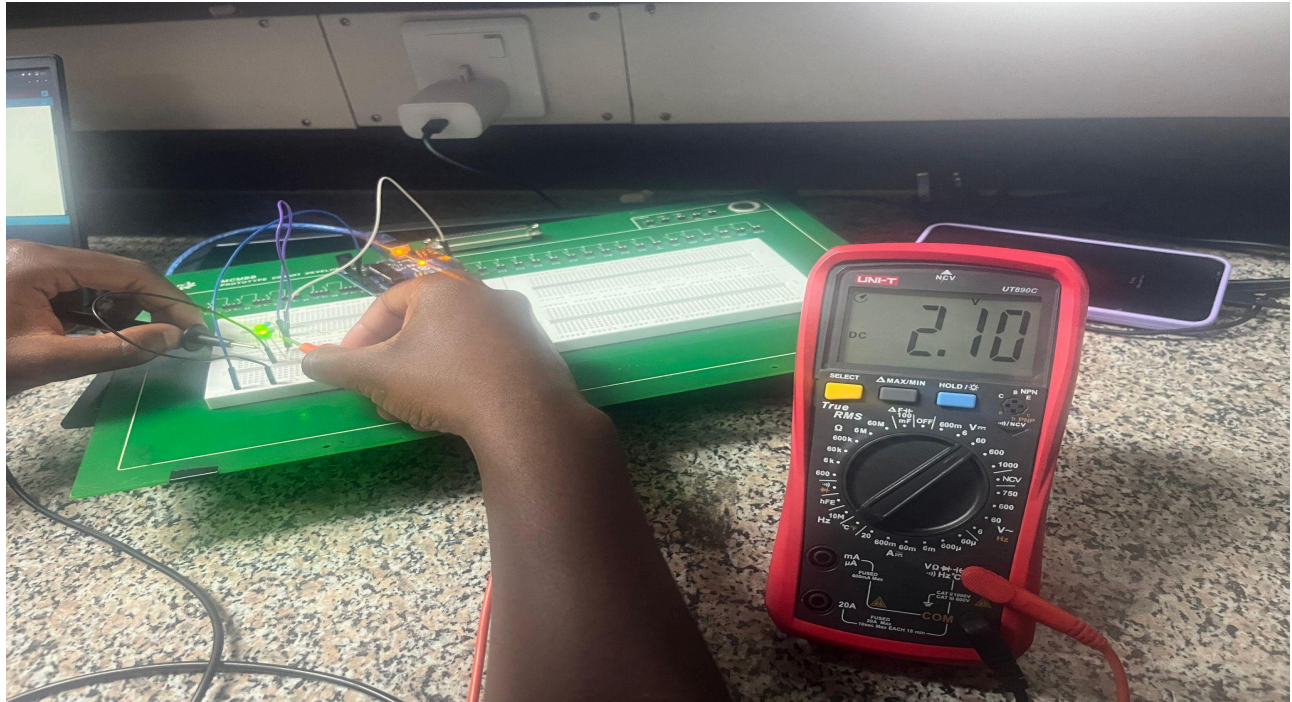

Voltage across Resistor 2:

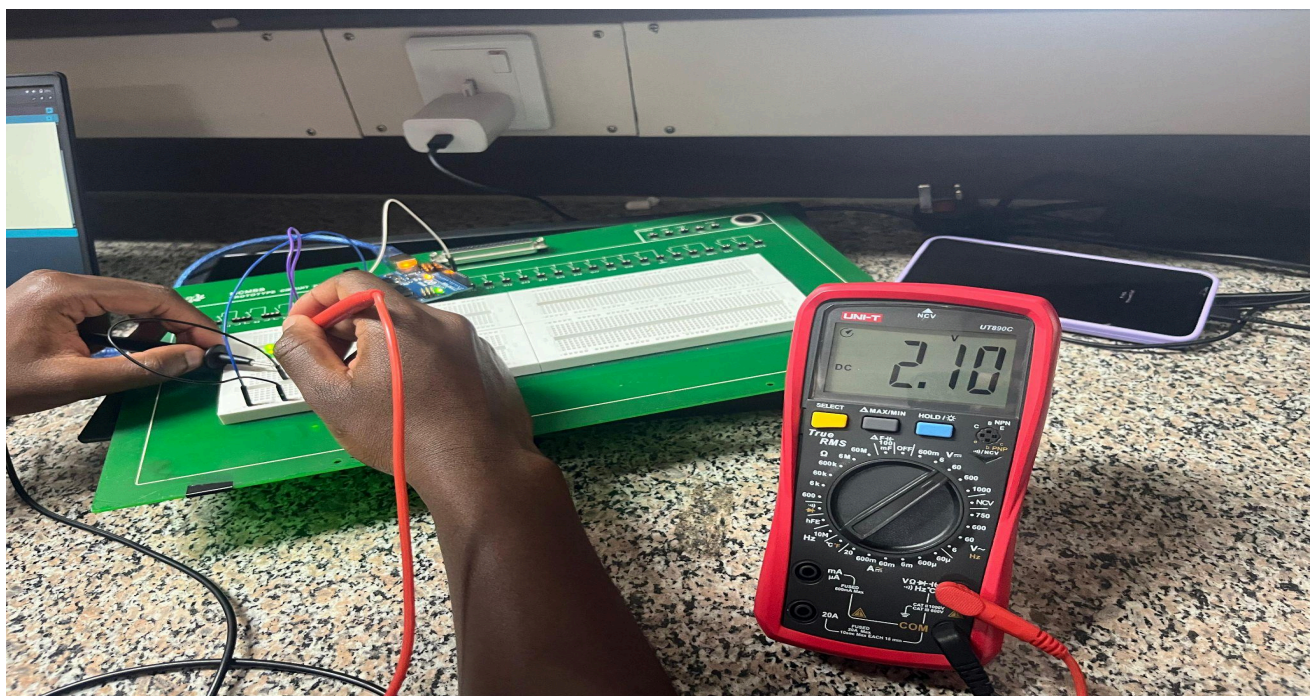

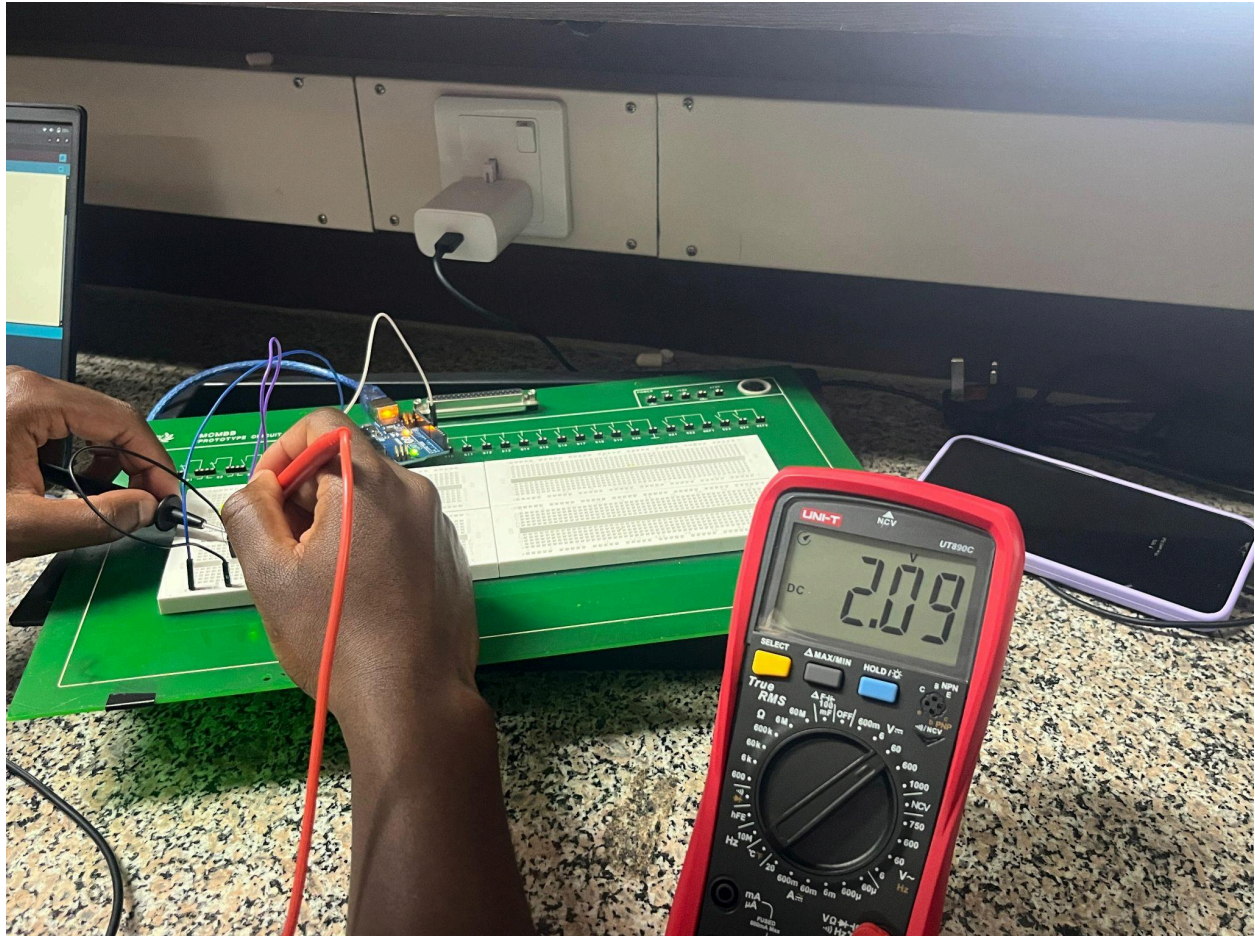Total Voltage Across the Circuit(Total Voltage = Voltage at R1 = Voltage at R2):



Group Photo

